


Signal Processing and Linear Systems 1

Circuits Review

Units and Ohm's Law

$$V=IR$$

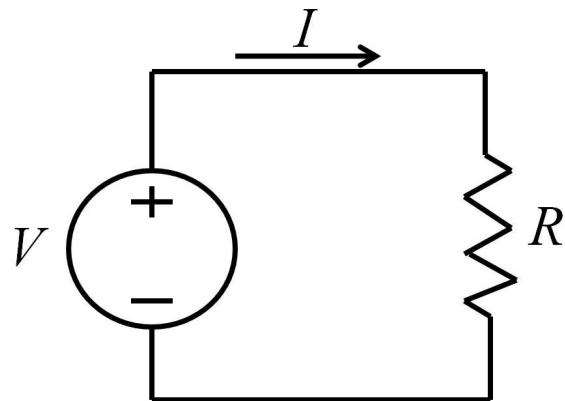
- Units
 - Voltage (V): volts (V) (= J/C)
 - Current (I): amps (A) (=C/s)
 - Resistance (R): ohms (Ω)



Units and Ohm's Law

$$V=IR$$

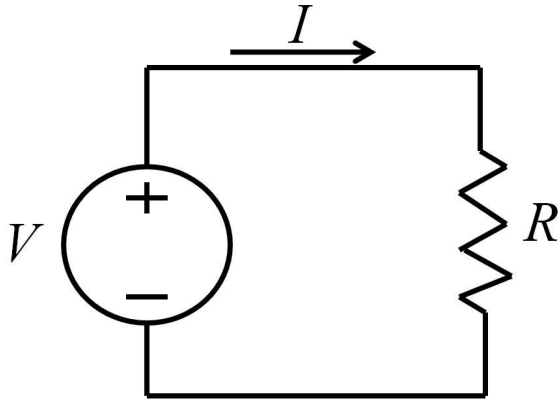
- Units
 - Voltage (V): volts (V) (= J/C)
 - Current (I): amps (A) (=C/s)
 - Resistance (R): ohms (Ω)
- Water Analogy
 - Voltage ~ water pressure
 - Current ~ flow rate
 - Resistance ~ pipe width



Units and Ohm's Law

$$V=IR$$


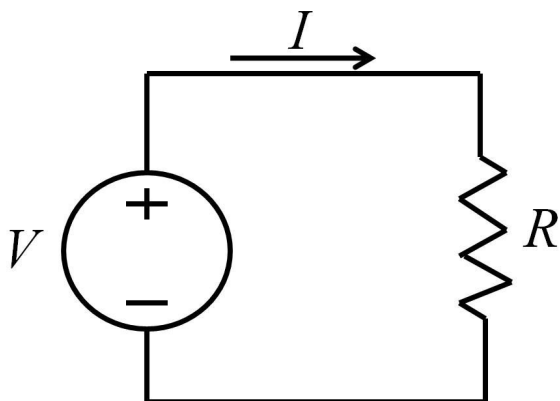
- Units
 - Voltage (V): volts (V) (= J/C)
 - Current (I): amps (A) (=C/s)
 - Resistance (R): ohms (Ω)
- Water Analogy
 - Voltage ~ water pressure
 - Current ~ flow rate
 - Resistance ~ pipe width
- Conventional Current
 - Current flows from high to low voltage by convention



Open and short

$$V=IR$$

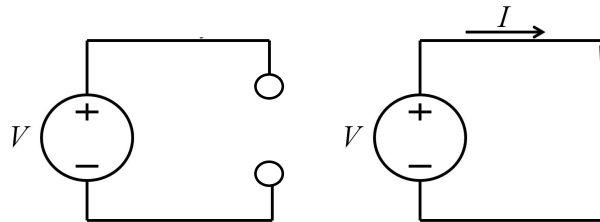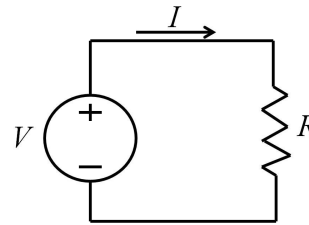
- When $R = \infty$, we have an open circuit
- When $R = 0$, we have a short



Kirchoff's Current Law (KCL)

$$\sum_{k=1}^n I_k = 0$$

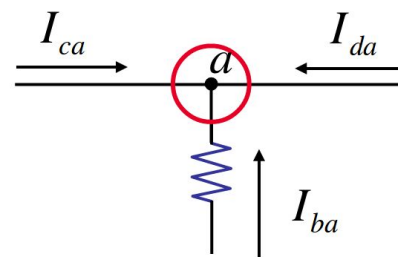- The sum of current into any node is zero
- Current flowing towards a node given positive sign, while current flowing away given negative sign
- This Law follows from the conservation of charge
- Water analogy: net water flowing into any point must be zero




$$I_{ca} + I_{da} + I_{ba} = 0$$

Kirchoff's Voltage Law (KVL)

$$\sum_{k=1}^n V_k = 0$$

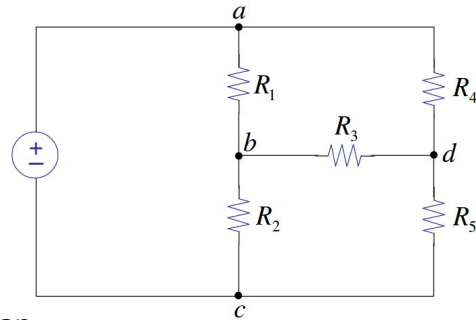
- The sum of voltages along and loop is zero
- Each voltage as you move along the loop can be positive or negative
- This Law follows from the conservation of energy



Kirchoff's Voltage Law (KVL)

$$\sum_{k=1}^n V_k = 0$$

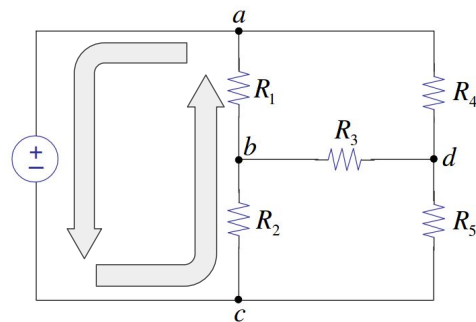- The sum of voltages along and loop is zero
- Each voltage as you move along the loop can be positive or negative
- This Law follows from the conservation of energy




$$v_{ac} + v_{cb} + v_{ba} = 0$$

Kirchoff's Voltage Law (KVL)

$$\sum_{k=1}^n V_k = 0$$

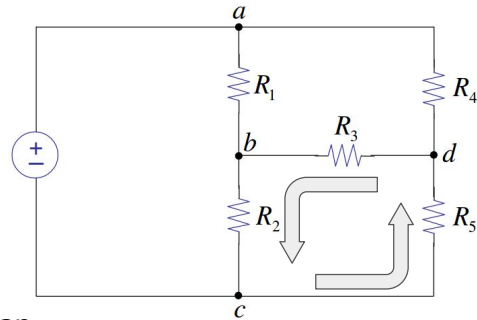- The sum of voltages along and loop is zero
- Each voltage as you move along the loop can be positive or negative
- This Law follows from the conservation of energy




$$V_{ac} + V_{cb} + V_{ba} = 0$$

$$V_{bc} + V_{cd} + V_{db} = 0$$

Kirchoff's Voltage Law (KVL)

$$\sum_{k=1}^n V_k = 0$$

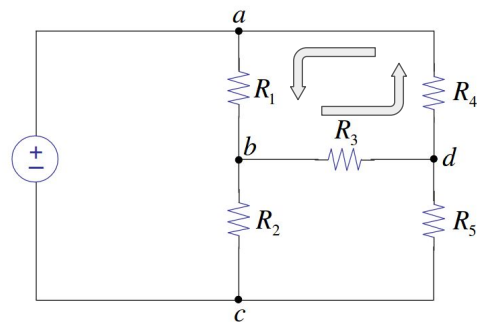- The sum of voltages along and loop is zero
- Each voltage as you move along the loop can be positive or negative
- This Law follows from the conservation of energy



$$V_{ac} + V_{cb} + V_{ba} = 0$$


$$V_{bc} + V_{cd} + V_{db} = 0$$

$$V_{ab} + V_{bd} + V_{da} = 0$$

Resistors in Series

$$R_{\text{eq}} = R_1 + R_2 + \dots + R_n$$


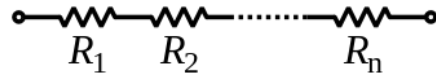
- The equivalent resistance of resistors connected in series is the sum of the individual resistances
- This rule follows from Ohm's law and KCL
 - A consequence of KCL is that portions of circuit that are in series must have the same current. Here, the current through each resistor must be equal.



Resistors in Parallel

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

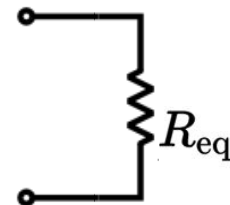
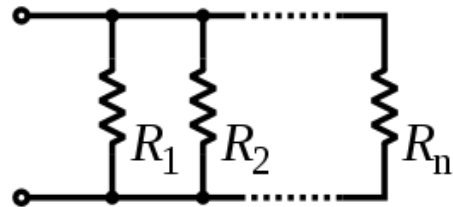
- The equivalent resistance of resistors connected in parallel is the harmonic mean of the individual resistances
- This rule follows from Ohm's law and KVL
 - A consequence of KVL is that portions of circuit that are in parallel must have the same voltage. Here, the voltage across each resistor must be equal.



Resistors in Parallel - Water Analogy


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

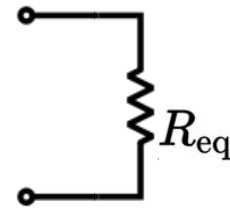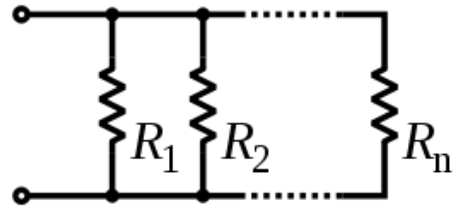- Imagine two water pipes in series, when very skinny (high resistance), one very wide (low resistance).
- The overall resistance will be determined by the wider pipe
- Most of the water (current) will flow through the wider pipe



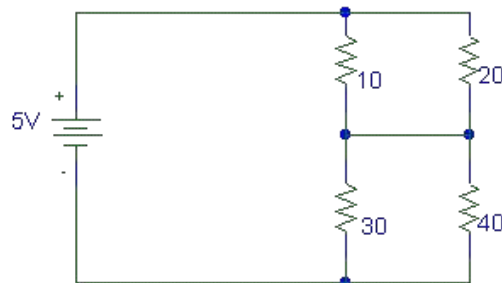
Example of Combining these Rules

- What is the equivalent resistance of the four resistors?
- What is the current flow through each resistor?
- (work out on board)



Voltage Divider

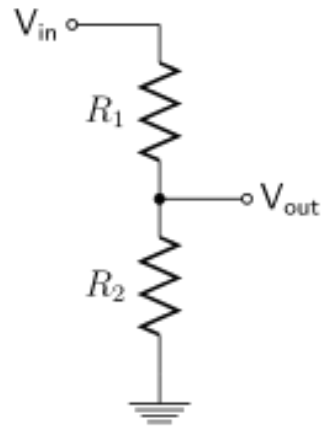
- What is V_{out} ? As function of V_{in} ?
- (work out on board)



Voltage Divider

- What is V_{out} ? As function of V_{in} ?
- Combined resistance is $R_1 + R_2$
- Thus, current is $I = V_{in} / (R_1 + R_2)$
- $V_{out} = I * R_2 = (V_{in} / (R_1 + R_2)) * R_2$
- $V_{out} / V_{in} = R_2 / (R_1 + R_2)$
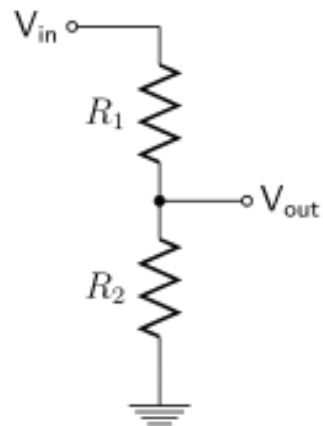
$$V_{out} = \frac{R_2}{R_1 + R_2} \cdot V_{in}$$



Resistors, Capacitors, and Inductors

Resistor



$$V = IR$$

- Physically, a resistor is usually a strip of partially insulative material

Capacitor



$$I = C \frac{dV}{dt}$$

- Physically, a capacitor is usually two parallel charged plates separated by an insulator

Voltage



$$V = L \frac{dI}{dt}$$

- Physically, an inductor is usually a coil of wire
- It opposes change in current

Impedances

- Capacitors and Inductors have a complex valued "resistance"

$$Z_C = \frac{1}{j\omega C} \text{ --- } \text{Capacitor}$$

$$Z_L = j\omega L \text{ --- } \text{Inductor}$$

$$Z_R = R \text{ --- } \text{Resistor}$$

where ω is the frequency

Impedances

- Capacitors and Inductors have a complex valued “resistance”
- This generalized notion of resistance is known as impedance.

$$Z_C = \frac{1}{j\omega C} \text{ --- } \text{Capacitor}$$

$$Z_L = j\omega L \text{ --- } \text{Inductor}$$

$$Z_R = R \text{ --- } \text{Resistor}$$

where ω is the frequency

Impedances

- Capacitors and Inductors have a complex valued “resistance”
- This generalized notion of resistance is known as impedance.
- Note limiting behavior
 - At high frequency capacitor become shorts and inductors opens
 - At low frequency capacitors become opens and inductors shorts

$$Z_C = \frac{1}{j\omega C} \text{ --- } \text{Capacitor}$$

$$Z_L = j\omega L \text{ --- } \text{Inductor}$$

$$Z_R = R \text{ --- } \text{Resistor}$$

where ω is the frequency

Impedances(cont'd)

- When resistors, capacitors, and inductors are combined in circuits their impedances are combined by same rules we saw for resistors.
- We will look at a example on the next slide



$$Z_C = \frac{1}{j\omega C} \quad \text{---||---} \quad \text{Capacitor}$$

$$Z_L = j\omega L \quad \text{---\textcircled{L}---} \quad \text{Inductor}$$

$$Z_R = R \quad \text{---\text{Z}---} \quad \text{Resistor}$$

RC Low-Pass Filter

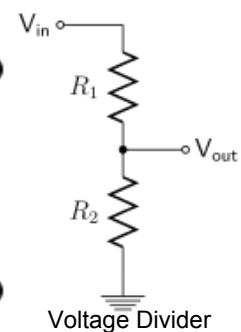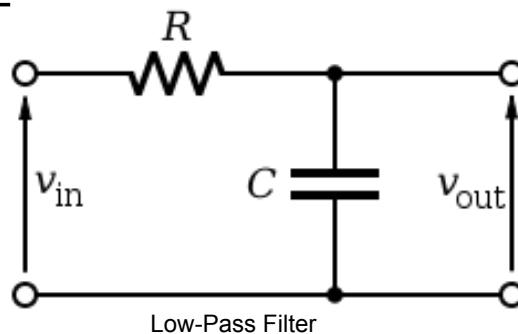- This RC circuit is the same as the voltage divider we saw earlier except that we are now replace resistances with impedances.
- V_{out}/V_{in} is known as the transfer function.



$$\frac{V_{out}}{V_{in}} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC} \quad V_{out} = \frac{R_2}{R_1 + R_2} \cdot V_{in}$$

RC Low-Pass Filter (cont'd)

- We can examine both the magnitude and the phase of this complex valued transfer function.

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + j\omega RC} = \frac{1}{1 + j\frac{\omega}{f_c}}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{f_c}\right)^2}} \quad f_c = \frac{1}{RC}$$

$$\angle\left(\frac{V_{out}}{V_{in}}\right) = -\angle\left(1 + j\frac{\omega}{f_c}\right) = -\arctan\left(\frac{\omega}{f_c}\right)$$

RC Low-Pass Filter (Cont'd)

- Recall that at low frequency a capacitor is like an open and at high frequency it is like a short. Let's check if this matches low pass behavior
- Indeed, if the capacitor is replaced with an open, $V_{out} = V_{in}$
- If the capacitor is replaced with a short, $V_{out} = 0$.
- This is often a good check to do.
- Exercise: What sort of filter will we get if we switch the place of the resistor and the capacitor? What will the transfer function be?

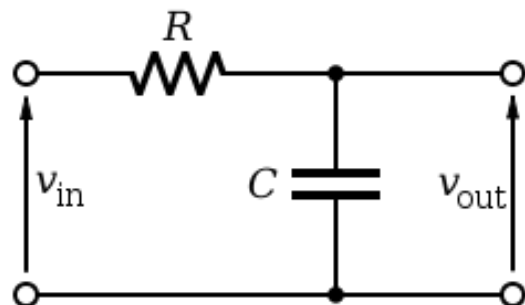


Image Credits

- Wikipedia
- [Calvin College](#)
- http://www.electronics-tutorials.ws/filter/filter_2.html
- MIT Open Courseware - 6.002 Prof. Anant Agarwal